

*TEMP 101 Circuits and Signals*

*Tutorial on RC Low Pass Filter*

*&*

*RC High Pass Filter*

*By*

*Tony Aby Varkey M*

*Assistant Professor*

*Dept. of ECE*

*Presidency University*

# Low Pass RC Filter

The cut off frequency is given as


$$f_c = \frac{1}{2\pi RC}$$

The magnitude response is given as

$$M = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

The phase response is
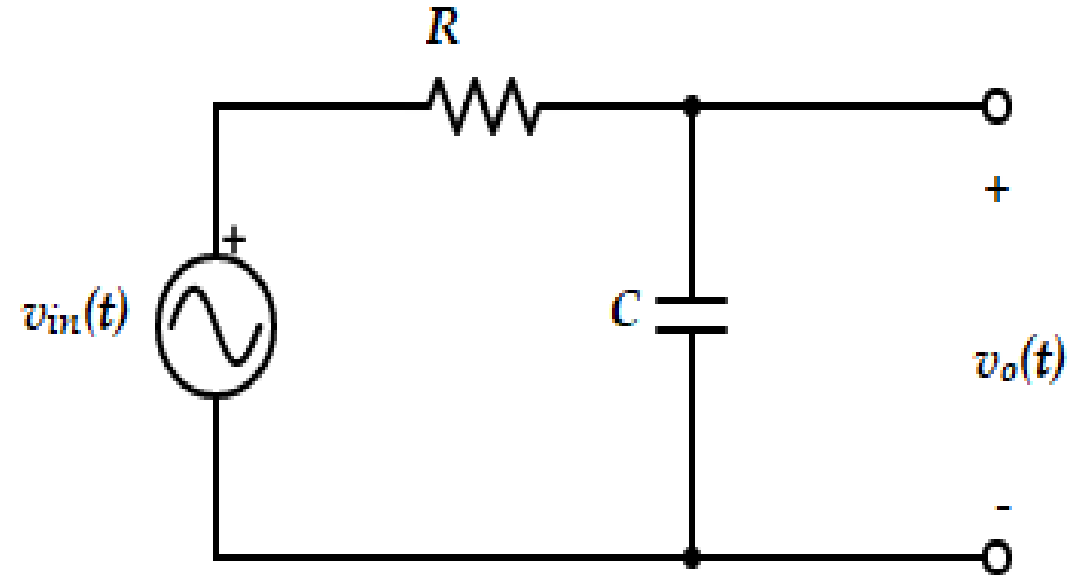
$$\phi = -\tan^{-1}\left(\frac{f}{f_c}\right)$$



## Question

Design a first order low pass filter RC filter for a cut off frequency of 1000 Hz. Evaluate the gain in dB and phase at the following frequencies

$f$	$0.01f_c$	$0.1f_c$	$0.2f_c$	$0.5f_c$	$0.7f_c$	$f_c$	$2f_c$	$5f_c$	$7f_c$	$10f_c$	$20f_c$	$100f_c$
-----	-----------	----------	----------	----------	----------	-------	--------	--------	--------	---------	---------	----------

### Answer:

The circuit diagram is shown

The cut off frequency is given as


$$f_c = \frac{1}{2\pi RC}$$

The required cut off frequency is

$$f_c = 1000 \text{ Hz}$$

So

$$\frac{1}{2\pi RC} = 1000$$

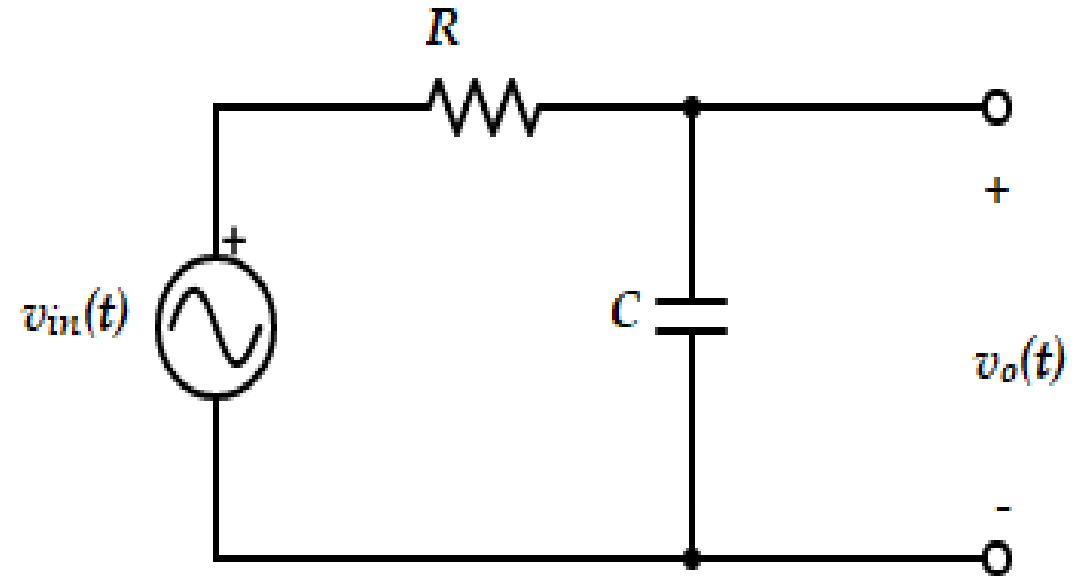

## Question

Design a first order low pass filter RC filter for a cut off frequency of 1000 Hz. Evaluate the gain in dB and phase at the following frequencies

$f$	$0.01f_c$	$0.1f_c$	$0.2f_c$	$0.5f_c$	$0.7f_c$	$f_c$	$2f_c$	$5f_c$	$7f_c$	$10f_c$	$20f_c$	$100f_c$
-----	-----------	----------	----------	----------	----------	-------	--------	--------	--------	---------	---------	----------

$$\frac{1}{2\pi RC} = 1000$$


Let  $C = 0.01 \mu F$

$$R = \frac{1}{2\pi f_c C}$$

$$R = \frac{1}{2\pi \times 1000 \times 0.01 \times 10^{-6}}$$

$$R = 15915.49\Omega$$

$$R = 15.915 k\Omega$$

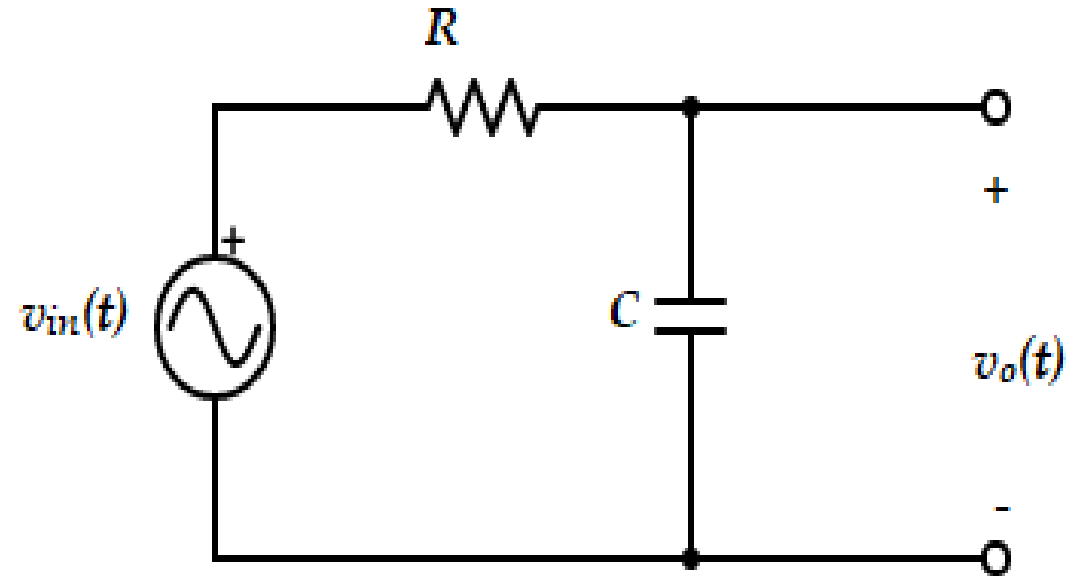

## Question

Design a first order low pass filter RC filter for a cut off frequency of 1000 Hz. Evaluate the gain in dB and phase at the following frequencies

$f$	$0.01f_c$	$0.1f_c$	$0.2f_c$	$0.5f_c$	$0.7f_c$	$f_c$	$2f_c$	$5f_c$	$7f_c$	$10f_c$	$20f_c$	$100f_c$
-----	-----------	----------	----------	----------	----------	-------	--------	--------	--------	---------	---------	----------

Gain is given as

$$M = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$f$	$0.01f_c$	$0.1f_c$	$0.2f_c$	$0.5f_c$	$0.7f_c$	$f_c$	$2f_c$	$5f_c$	$7f_c$	$10f_c$	$20f_c$	$100f_c$
$M$	1	0.995	0.9806	0.8944	0.8192	0.7071	0.4472	0.1961	0.1414	0.0995	0.0499	0.01

## Question

Design a first order low pass filter RC filter for a cut off frequency of 1000 Hz. Evaluate the gain in dB and phase at the following frequencies


$f$	$0.01f_c$	$0.1f_c$	$0.2f_c$	$0.5f_c$	$0.7f_c$	$f_c$	$2f_c$	$5f_c$	$7f_c$	$10f_c$	$20f_c$	$100f_c$
-----	-----------	----------	----------	----------	----------	-------	--------	--------	--------	---------	---------	----------

Gain in dB is given as


$$M_{dB} = 20 \cdot \log_{10}(M)$$

$f$	$0.01f_c$	$0.1f_c$	$0.2f_c$	$0.5f_c$	$0.7f_c$	$f_c$	$2f_c$	$5f_c$	$7f_c$	$10f_c$	$20f_c$	$100f_c$
$M$	1	0.995	0.9806	0.8944	0.8192	0.7071	0.4472	0.1961	0.1414	0.0995	0.0499	0.01
$M_{dB}$	0	-0.04	-0.17	-0.97	-1.73	-3.01	-6.99	-14.15	-16.99	-20.04	-26.04	-40

# Magnitude Response

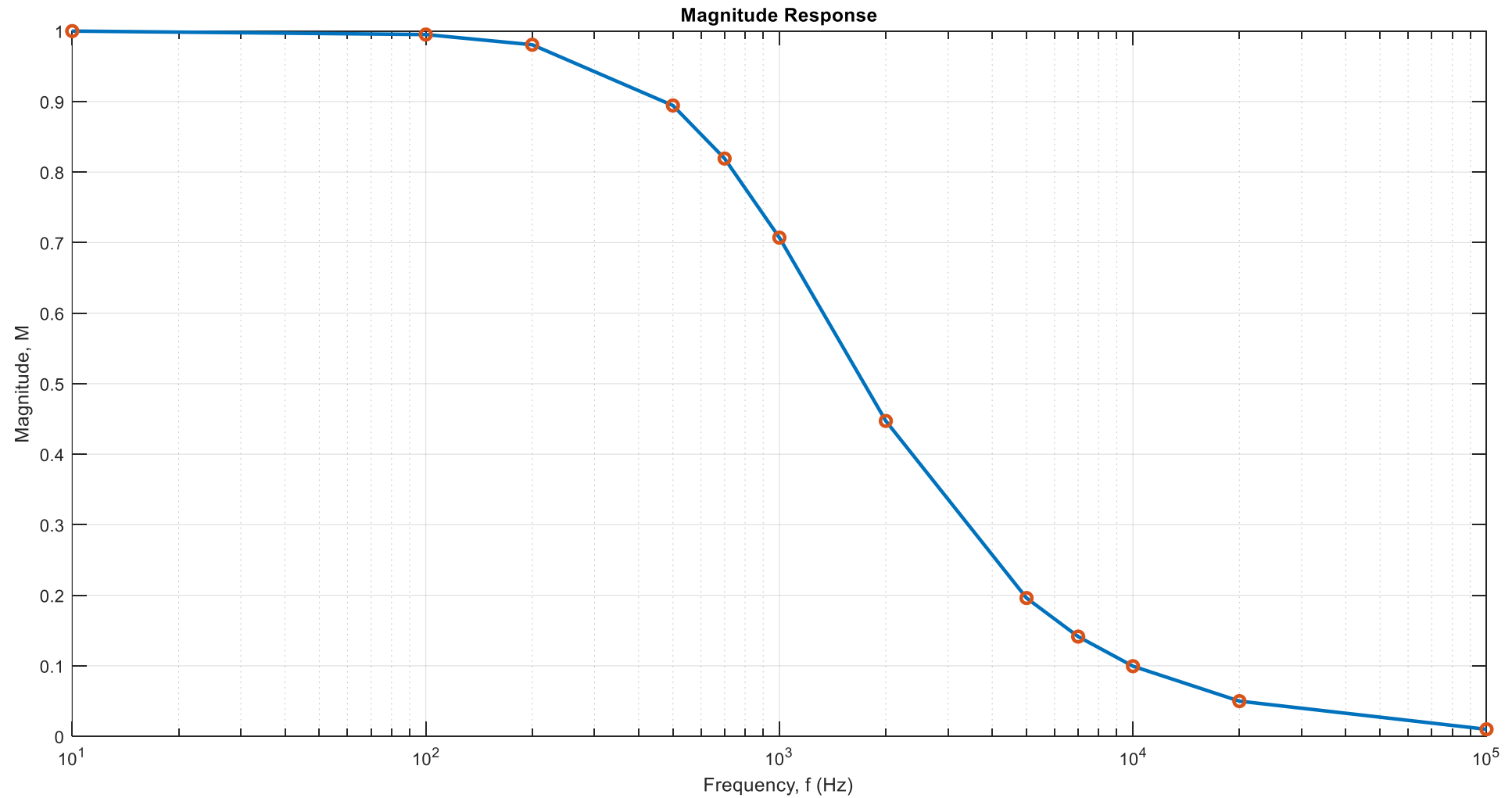


# Magnitude Response

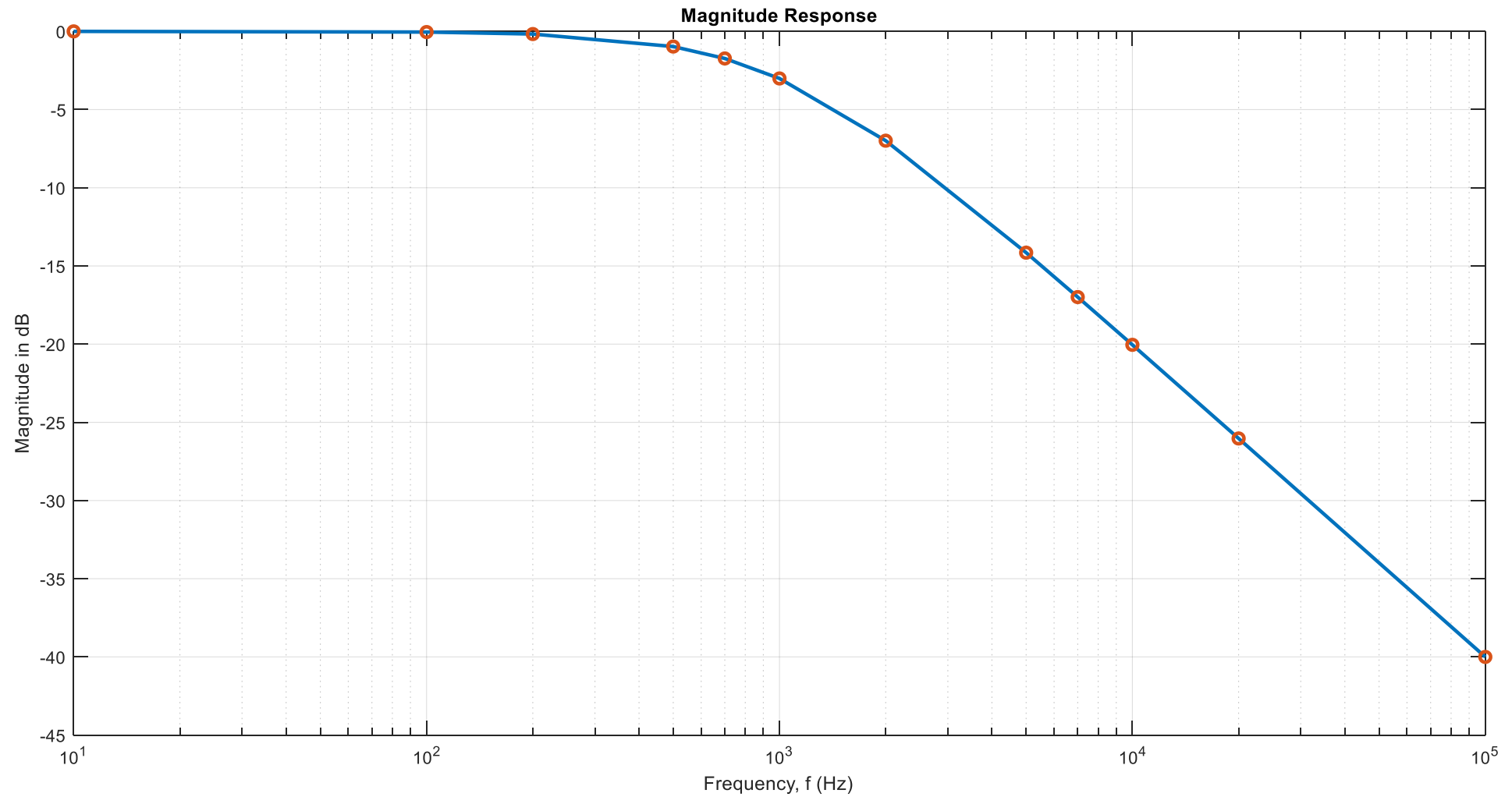



# High Pass RC Filter

The circuit diagram is shown

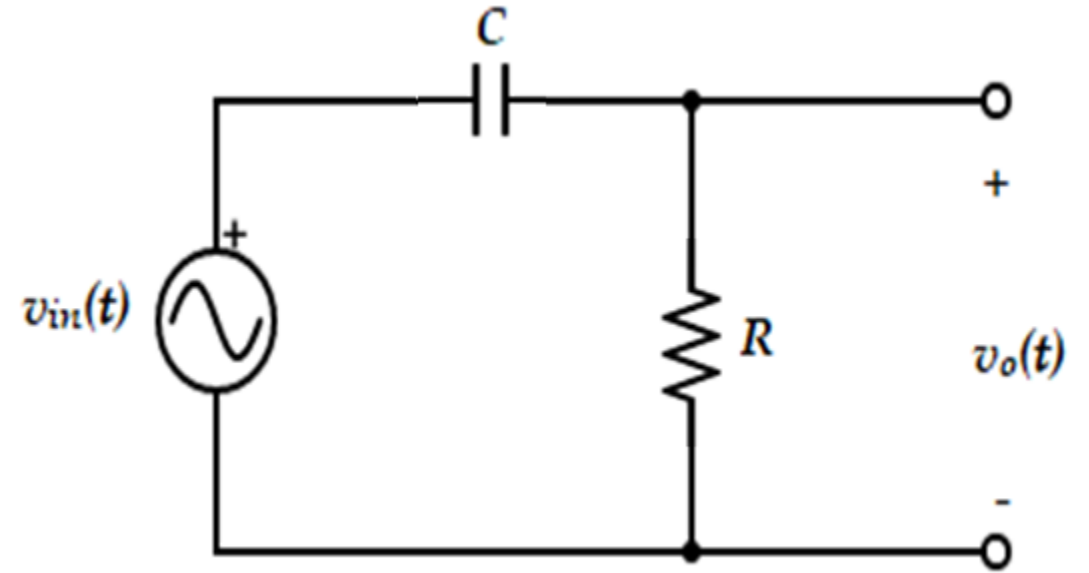

# High Pass RC Filter

The circuit diagram of a RC high pass filter is shown

Let  $i(t)$  be the current flowing through the circuit



Impedance of the capacitor is

$$Z_C(j\omega) = \frac{1}{j\omega C}$$

We can draw the circuit diagram in the frequency domain as follows

According to Voltage division rule, the voltage across the capacitor or the output voltage will be
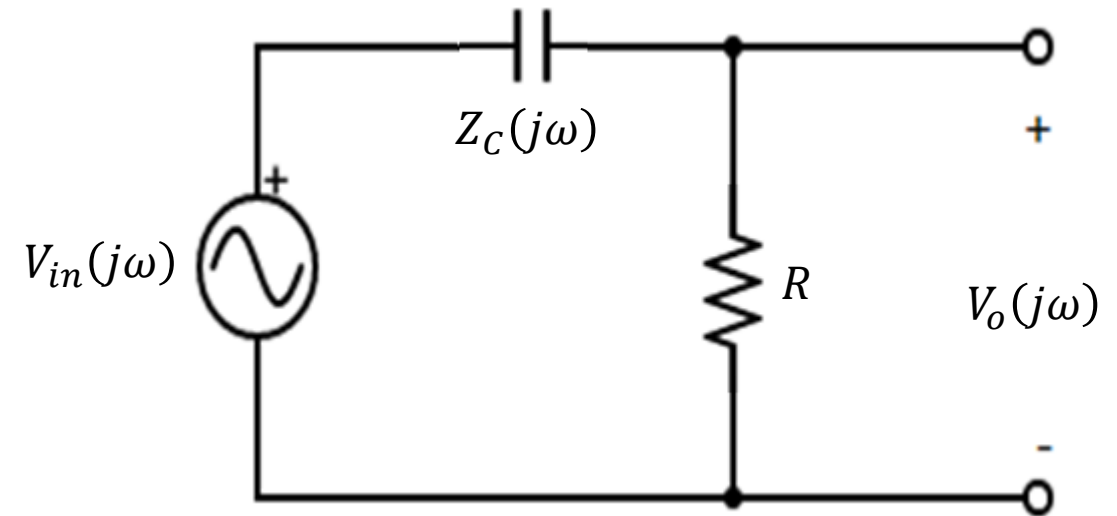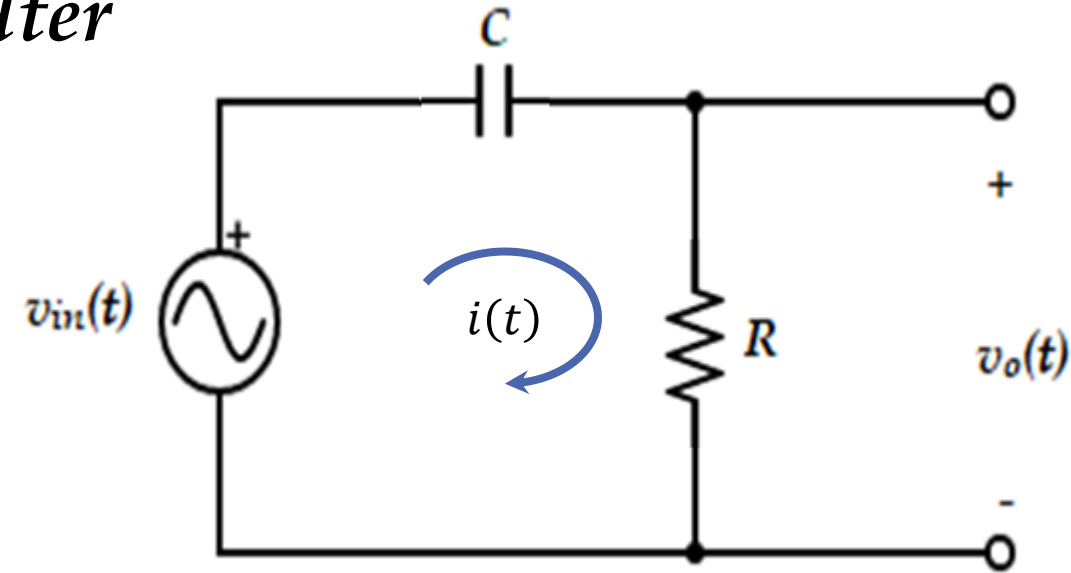
$$V_o(j\omega) = \frac{R}{R + Z_C(j\omega)} \times V_{in}(j\omega)$$



# High Pass RC Filter

$$V_o(j\omega) = \frac{R}{R + Z_C(j\omega)} \times V_{in}(j\omega)$$

$$\frac{V_o(j\omega)}{V_{in}(j\omega)} = \frac{R}{R + Z_C(j\omega)}$$

Substituting for  $Z_C(j\omega)$ , we get

$$\frac{V_o(j\omega)}{V_{in}(j\omega)} = \frac{R}{R + \frac{1}{j\omega C}}$$


$$\frac{V_o(j\omega)}{V_{in}(j\omega)} = \frac{j\omega RC}{j\omega RC + 1}$$

What is  $\frac{V_o(j\omega)}{V_{in}(j\omega)}$ ?

It is the frequency response. So

$$H(j\omega) = \frac{j\omega RC}{j\omega RC + 1}$$

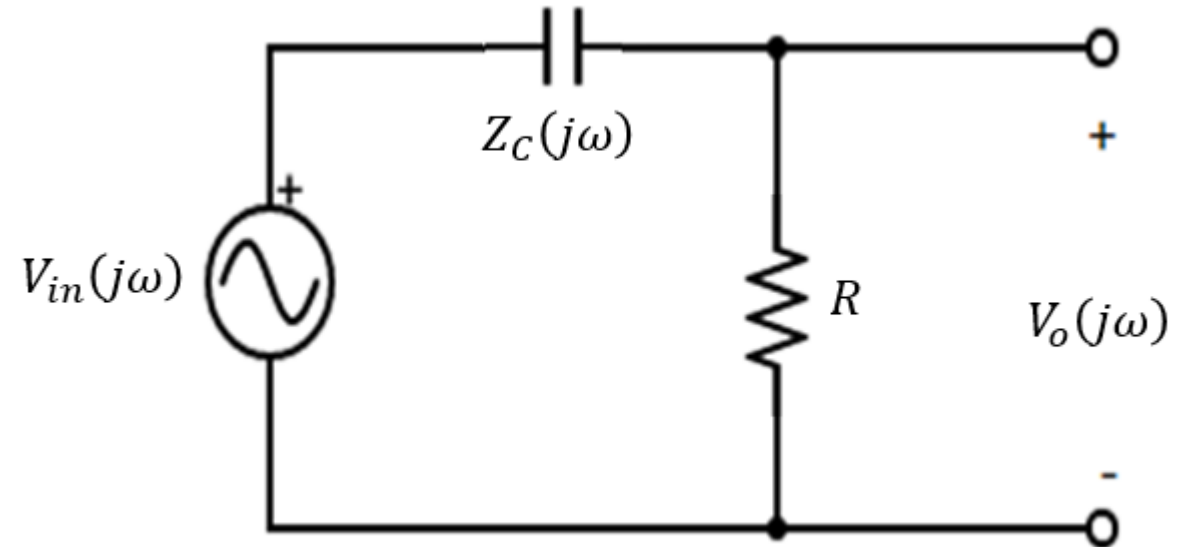Where  $H(j\omega)$  is the frequency response



# High Pass RC Filter

$$H(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

What is  $\omega$ ?


$$\omega = 2\pi f$$

So

$$H(f) = \frac{j2\pi f RC}{1 + j2\pi f RC}$$

$$H(f) = \frac{1}{\frac{1}{j2\pi f RC} + 1}$$
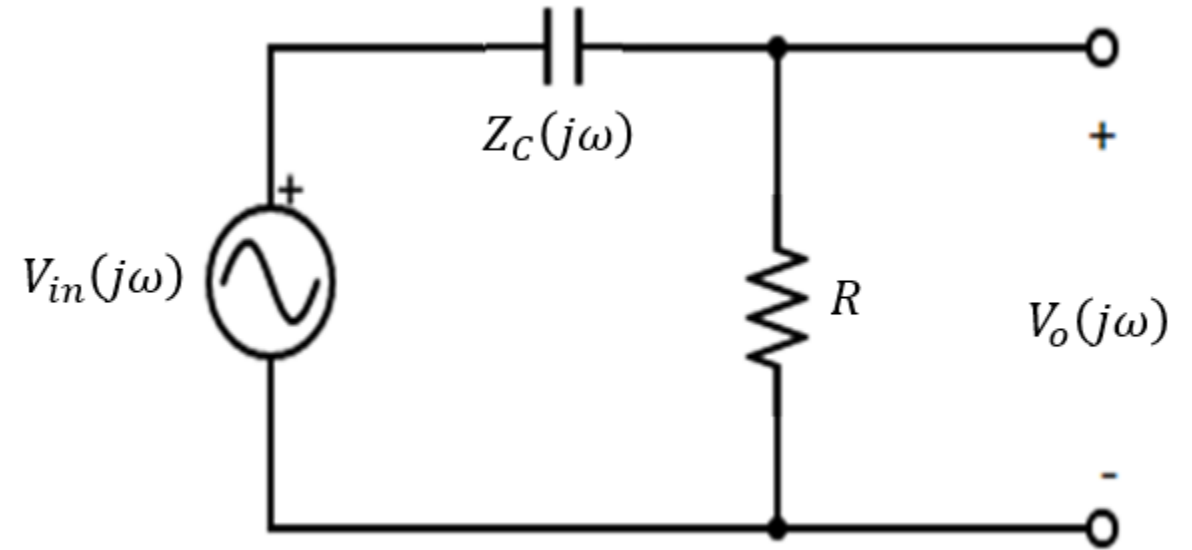
$$H(f) = \frac{1}{1 - j\frac{1}{2\pi f RC}}$$



Let

$$f_c = \frac{1}{2\pi RC}$$

Then

$$H(f) = \frac{1}{1 - j\frac{f_c}{f}}$$

# High Pass RC Filter

$$H(f) = \frac{1}{1 - j \frac{f_c}{f}}$$

The magnitude response is

$$M = |H(f)| = \left| \frac{1}{1 - j \frac{f_c}{f}} \right|$$


$$M = \frac{1}{\sqrt{1 + \left(\frac{f_c}{f}\right)^2}}$$

The phase response is

$$\phi = \angle H(f)$$

$$\phi = 0 - \tan^{-1} \left( \frac{f_c}{f} \right)$$
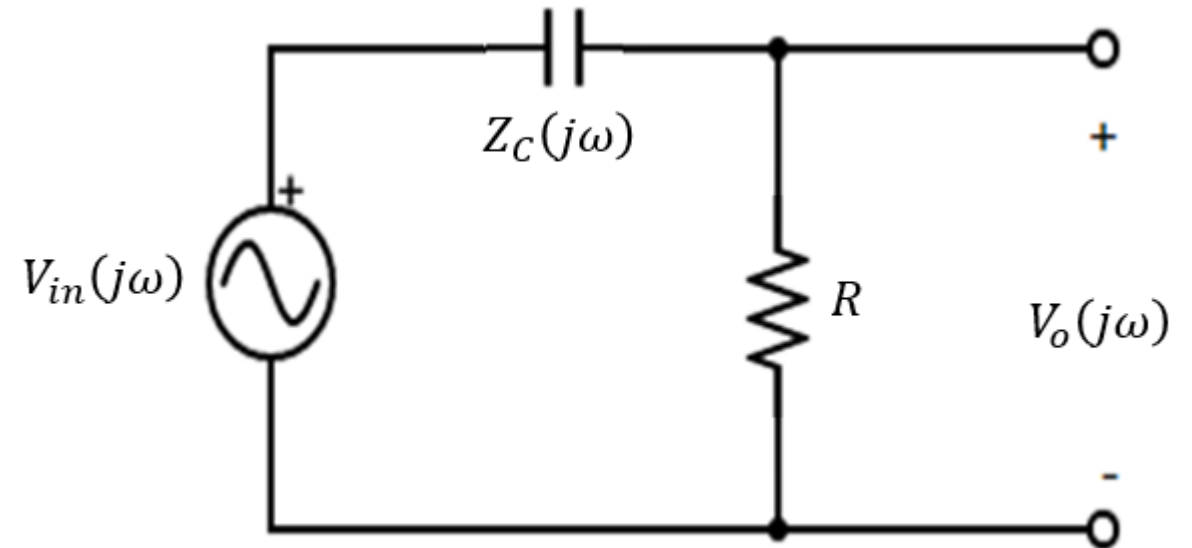
$$\phi = \tan^{-1} \left( \frac{f_c}{f} \right)$$



*Thank You*